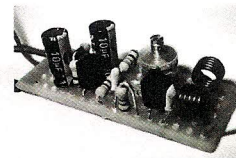




İZMİR UNIVERSITY OF ECONOMICS
Department of Electrical and Electronics Engineering
EEE 331 Analog Electronics
Fall 2015/2016



FINAL EXAM

Jan 5, 2016

150 min

SOLUTIONS

INSTRUCTIONS


- | | |
|--|--|
| <p> Read all of the instructions and all of the questions before beginning the exam.</p> <p> There are 5 questions on this exam, totaling 100 points. The credit for each problem is given to help you allocate your time accordingly.</p> <p> Do not spend all your time on one problem and on one part and attempt to solve all of them.</p> <p> Calculators are allowed, but borrowing is not allowed.</p> <p> Your mobile phones must be turned off during the exam.</p> | <p> Turn in the entire exam, including this cover sheet. You must show your work for all problems to receive full credit; simply providing answers will result in only partial credit, even if the answers are correct.</p> <p> Please indicate the number of page where your work is to be continued.</p> <p> Put your name on any additional material that you submit.</p> <p> Be sure to provide units where necessary.</p> |
|--|--|

	Question	Points	Grade
Last Name :.....	1	20	
Name :.....	2	20	
Section :.....	3	20	
Student No :.....	4	20	
	5	20	
	TOTAL	100	

The basic equations of the output characteristics of an NMOS transistor

V_{GS}	V_{DS}	I_D
i) $V_{GS} < V_{Tn}$	-	0
ii) $V_{GS} > V_{Tn}$	a) $V_{DS} < V_{GS} - V_{Tn}$	$K_n [2(V_{GS} - V_{Tn})V_{DS} - V_{DS}^2]$
	b) $V_{GS} - V_{Tn} \leq V_{DS}$	$K_n (V_{GS} - V_{Tn})^2$
where $K_n = \frac{K'_n}{2} \left(\frac{W}{L} \right)$ and $K'_n = \mu_n C_{ox}$		

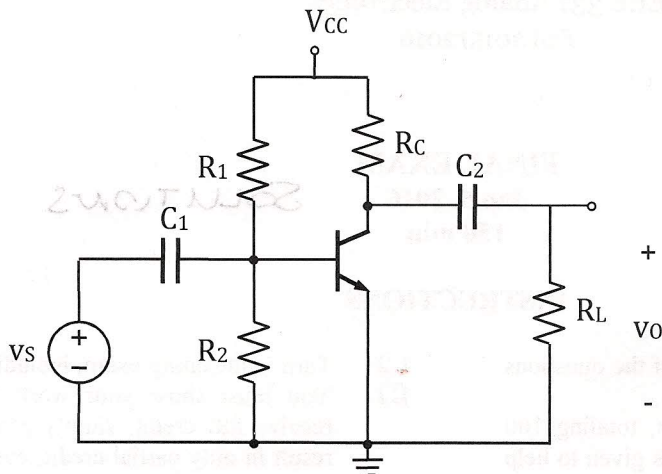Q1. (20 pts) Consider the following BJT amplifier.



Circuit Parameters



$V_{CC} = 15 \text{ V}$
 $R_1 = 400 \text{ k}\Omega$
 $R_2 = 220 \text{ k}\Omega$
 $R_C = 2 \text{ k}\Omega$
 $R_L = 40 \text{ k}\Omega$
 $C_1 = 50 \text{ }\mu\text{F}$
 $C_2 = 50 \text{ }\mu\text{F}$

Transistor Parameters



$V_{BE(ON)} = 0.7 \text{ V}$
 $V_T = 26 \text{ mV}$
 $\beta = 100$
 $V_A = \infty$

- Determine the small signal parameters and draw the low frequency small signal model.
- Determine the lower corner frequency.
- Find the midband voltage gain.
- Plot the low frequency magnitude response.

$|A|_{\text{dB}}, \text{ dB}$

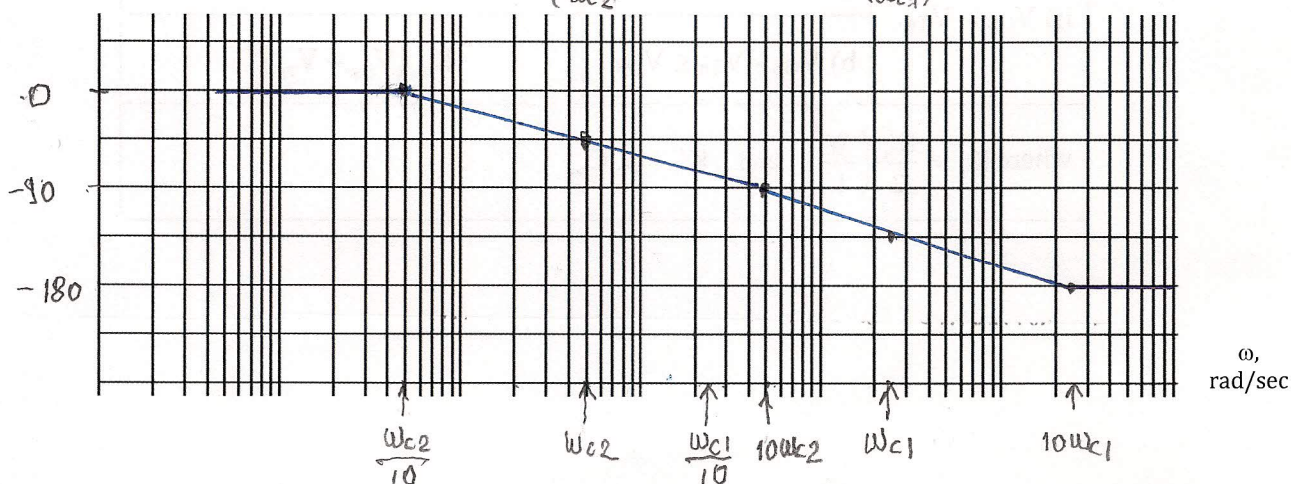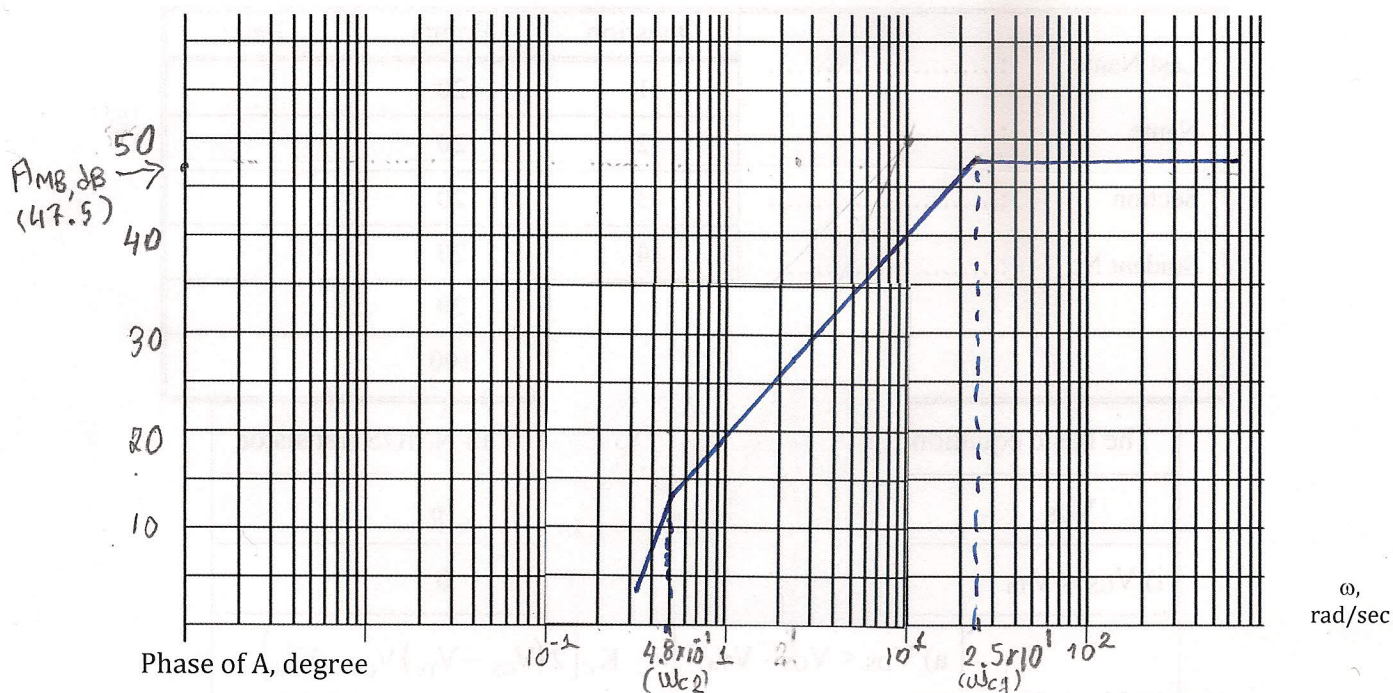

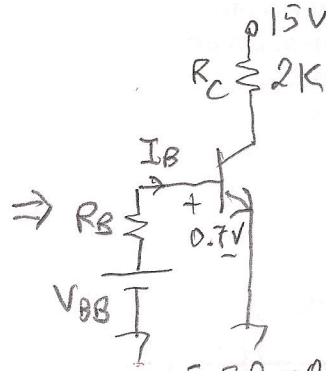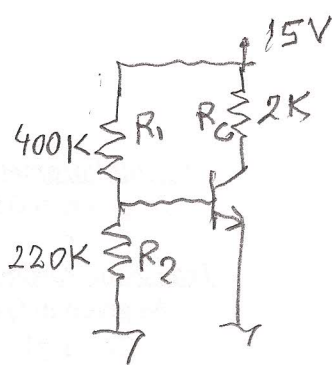(a) To determine small signal parameters, DC analysis is needed.



$$V_{BB} = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{220}{620} \cdot 15V$$

$$= 5.32V$$

$$R_B = R_1 \parallel R_2 = 141.9K$$


$$I_{BQ} = \frac{V_{BB} - V_{BE(ON)}}{R_B} = \frac{5.32 - 0.7}{141.9} = 32.56 \mu A \Rightarrow I_{CQ} = 3.256 mA$$

$$V_{CEQ} = V_{CC} - R_C I_{CQ} = 8.49V \quad (V_{CEQ} > V_{CE(SAT)} \text{ - Active})$$

$$r_{\pi} = \frac{V_T}{I_{BQ}} = \frac{26 mA}{32.56 \mu A} \approx 0.8K \Rightarrow g_m = \frac{\beta}{r_{\pi}} = \frac{100}{0.8K} = 125 mS$$

$$r_o = \infty$$

Low frequency small signal model :

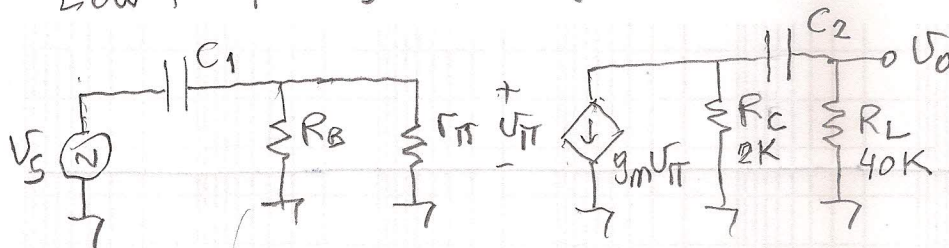

$$R'_L = R_C \parallel R_L = 1.9K$$

Two poles :

$$\omega_{c1} = \frac{1}{R_{eq1} C_1} ; R_{eq1} = R_B \parallel r_{\pi} = 141.9K \parallel 0.8K \approx 0.8K$$

$$\omega_{c1} = \frac{1}{(0.8K)(50\mu F)} = 25 \text{ rad/sec} = 2.5 \times 10^1 \text{ rad/sec}$$

$$\omega_{c2} = \frac{1}{R_{eq2} C_2} ; R_{eq2} = R_C + R_L = 42K$$

$$\omega_{c2} = \frac{1}{(42K)(50\mu F)} = 0.48 \text{ rad/sec} = 4.8 \times 10^{-1} \text{ rad/sec corner}$$

Midband gain =

$$V_{\pi} = V_S ; V_O = -g_m (R_C \parallel R_L) V_{\pi} = -(125 mS)(1.9K) = -237.5 V_S$$

$$A_V = -237.5 \Rightarrow A_{MB, dB} = 47.5 dB$$

$$A(j\omega) = \left(\frac{j\omega}{j\omega + \omega_{c1}} \right) \left(\frac{j\omega}{j\omega + \omega_{c2}} \right) A_{MB} = \frac{\omega^2 (237.5)}{(j\omega + \omega_{c1})(j\omega + \omega_{c2})}$$


i. Magnitude plot with two poles.

$$ii. \theta(j\omega) = -\tan^{-1}\left(\frac{\omega}{\omega_{c1}}\right) - \tan^{-1}\left(\frac{\omega}{\omega_{c2}}\right)$$

plots are on the upper page.

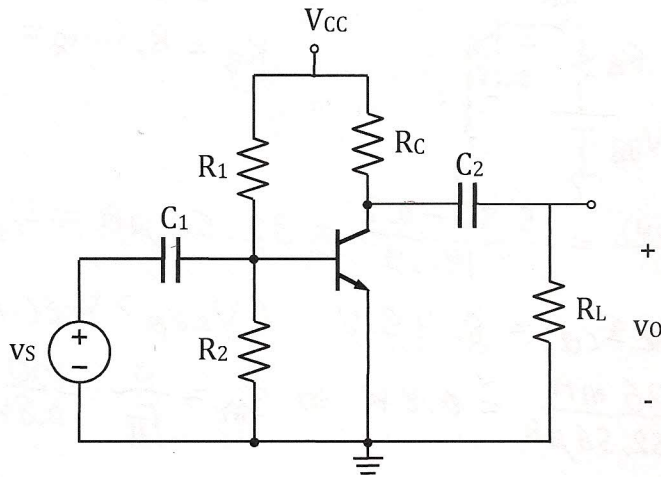Q2. (20 pts) Consider the BJT amplifier circuit given in Question 1 above.

- Draw the high-frequency equivalent circuit.
- Simplify the high-frequency equivalent circuit.
- Determine the higher corner frequency.
- Plot the overall frequency response.



Circuit Parameters


As given in Q1.

Transistor Parameters


As given in Q1.

$C_\pi = 1 \text{ pF}$

$C_\mu = 1 \text{ pF}$

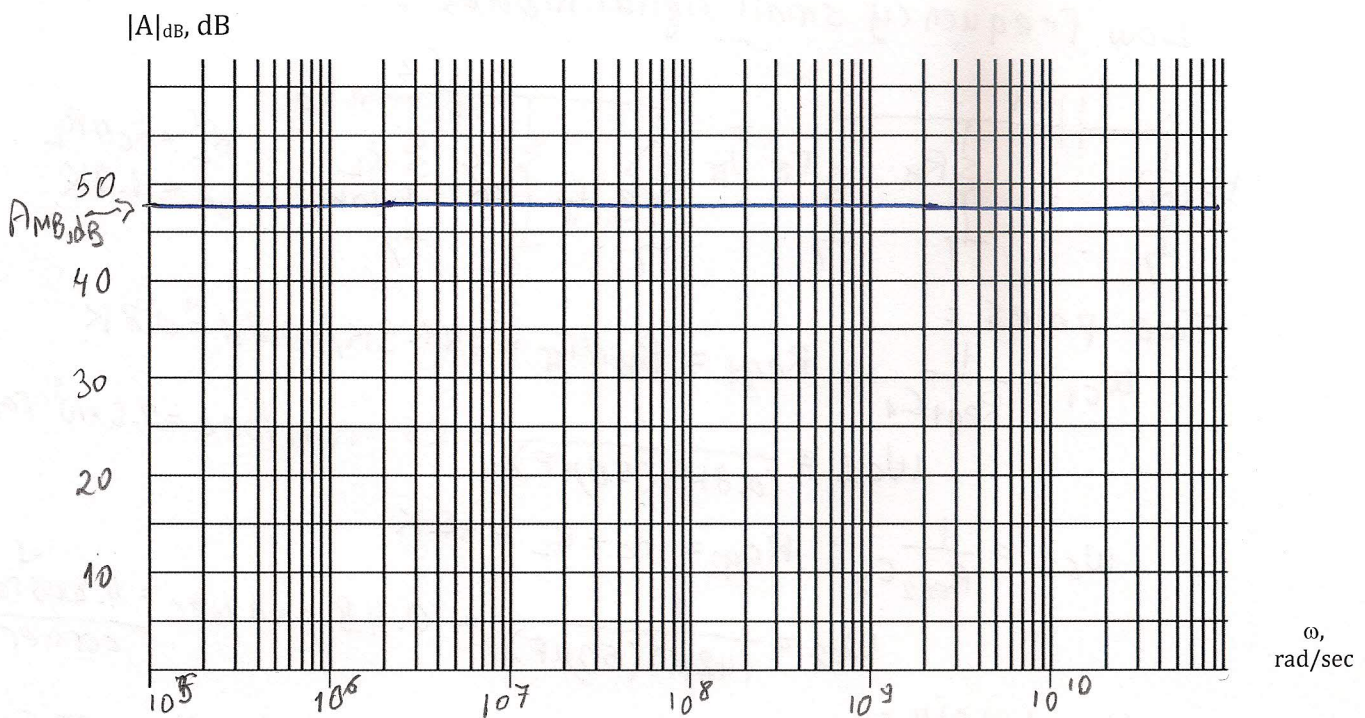

Phase of A, degree

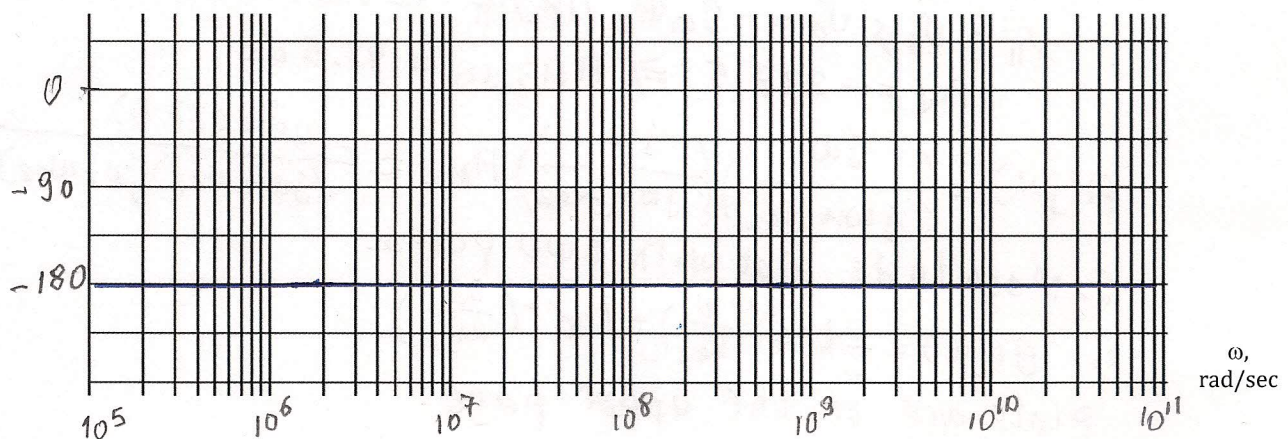


(i) From A_1 :

$$g_m = 125 \text{ mS}$$

$$A_{MB} = -237.5$$

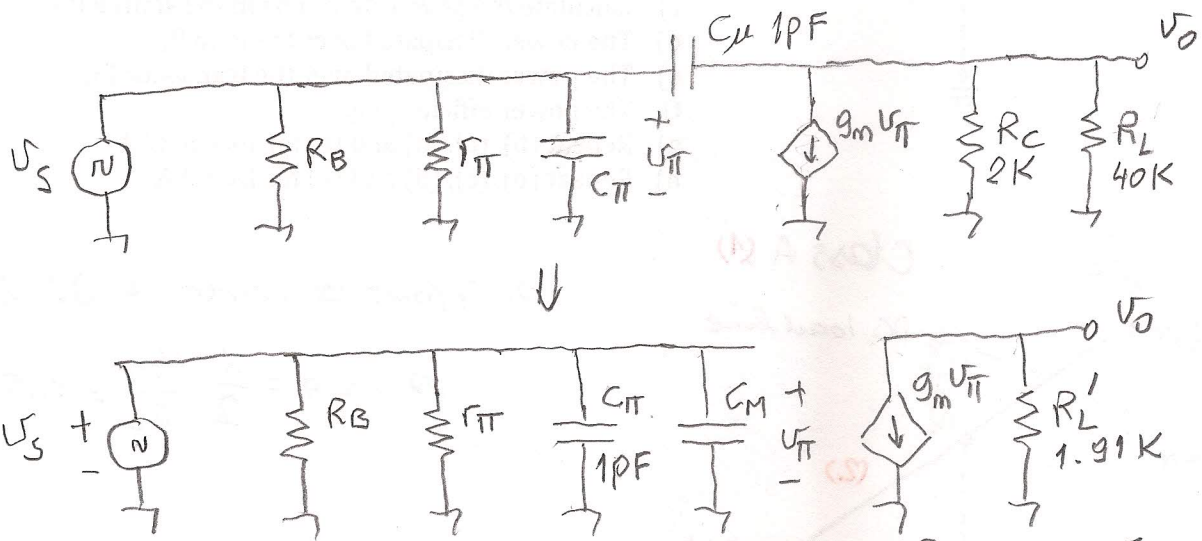High frequency small signal model
(External capacitors C_1 & C_2 are short)



$$C_M = C_{\mu}(1 + g_m R'_L) = 1 \text{ pF} [1 + (125)(1.91)] = 239.6 \text{ pF}$$

$$C_T = C_{\pi} + C_M = 240.6 \text{ pF}$$

In the high frequency region = (with single pole)

$$A(j\omega) = \frac{1}{1 + j \frac{\omega}{\omega_H}} \cdot A_{MB} =$$

$$A_{MB} = -237.5$$


$$\omega_H = \frac{1}{R_{eq} C_T} ; R_{eq} = 0 \text{ (since } V_S \text{ is short)}$$

then $\omega_H = \infty$ and $A(j\omega)$ reduces to

$$A(j\omega) = -237.5$$

$$\theta(j\omega) = -180^\circ$$

Q3. (20 pts)

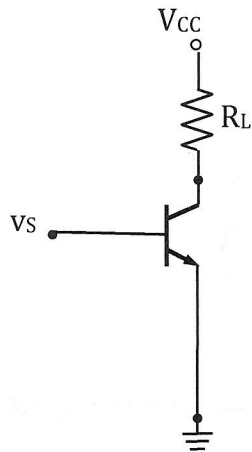

For the power amplifier given with


$$V_{CC} = 15 \text{ V}, R_L = 15 \Omega \text{ and } V_{CE(SAT)} = 0 \text{ V.}$$

- Draw the DC load line and determine the class of the power amplifier.
- Determine I_{CQ} assuming the Q-point is at the center of the DC load line and

Now consider

$$i_c(t) = I_{CQ} + I_{CP} \sin \omega t \text{ and } I_{CP} = 0.5 \text{ A.}$$

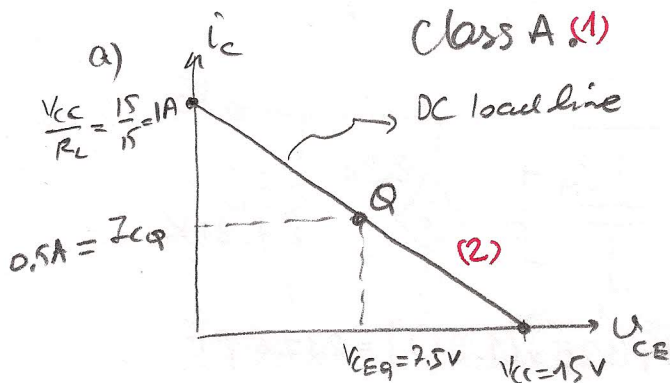- Calculate the power driven from the source P_{CC} ,
- The power dissipated over the load R_L ,
- The power dissipated over the transistor P_T ,
- The power efficiency η .
- Repeat (b), (c), (d) and (e) for $I_{CP} = 0.25 \text{ A}$.
- Repeat (b), (c), (d) and (e) for $I_{CP} = 0 \text{ A}$.



b) Q point @ center of DC load line

$$\Rightarrow I_{CQ} = \frac{1}{2} \frac{V_{CC}}{R_L} = 0.5 \text{ A. (1)}$$

$$c) P_{CC} = V_{CC} \cdot I_{CQ} = (15)(0.5) = 7.5 \text{ W (2)}$$

$$d) P_{L,DC} = R_L \cdot I_{CQ}^2 = (15)(0.5)^2 = 3.75 \text{ W (2)}$$

$$P_{L,AC} = \frac{1}{2} R_L I_{CP}^2 = \frac{1}{2} (15)(0.5)^2 = 1.875 \text{ W (2)}$$

$$e) P_T = P_{CC} - P_L = 7.5 - 3.75 - 1.875 = 1.875 \text{ W (2)}$$

$$f) \eta = \frac{P_{L,AC}}{P_{CC}} = \frac{1.875}{7.5} = 25\% \rightarrow \text{(highest power efficiency achievable in Class A power amps) (2)}$$

$$g) P_{L,AC} = \frac{1}{2} (15)(0.25)^2 = 0.469 \text{ W}$$


$$P_T = 7.5 - 3.75 - 0.469 = 3.28 \text{ W (3)}$$

$$\eta = \frac{0.469}{7.5} = 0.0625 = 6.25\%$$

h) $P_{L,AC} = 0 \text{ W}$

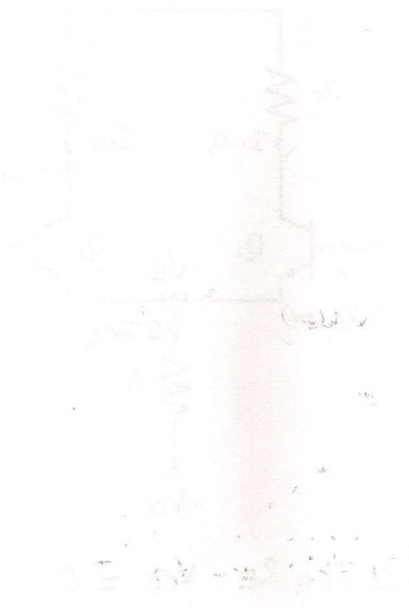
(3) $P_T = 7.5 - 3.75 = 3.75 \text{ W} \rightarrow$ highest transistor power
(used to select the transistor)

$\eta = 0\% \rightarrow$ lowest power efficiency.



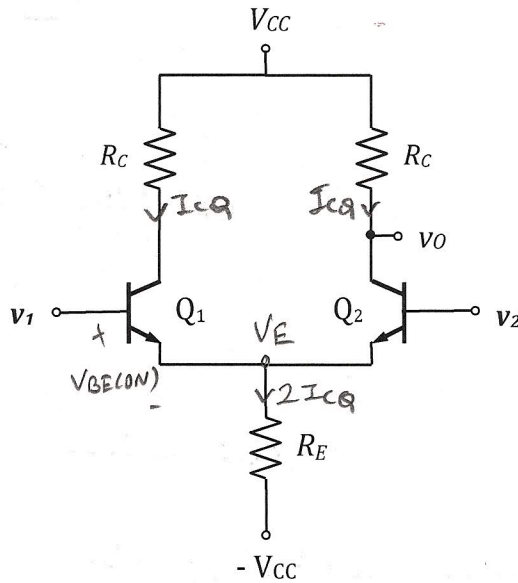Q4. (20 pts) Consider the differential amplifier given below. The output v_o is taken from the collector of Q_2 .

- Determine the value of R_E to set I_{CQ} as given below. (Check whether the transistors are in forward active or not.)
- Determine the DC value of the output voltage V_{OQ} .
- Find the differential-mode gain $A_{dm} = v_o/v_{dm}$.
- Find the common-mode gain $A_{cm} = v_o/v_{cm}$.
- Find CMRR.
- If $v_1 = 2 \sin(2\pi \cdot 75t) + 0.2 \sin(2\pi \cdot 1000t)$ volts, and $v_2 = 2 \sin(2\pi \cdot 75t) - 0.2 \sin(2\pi \cdot 1000t)$ volts, find the total voltage v_o .



Circuit Parameters

$$V_{CC} = 12 \text{ V}$$

$$R_C = 2 \text{ K}$$

$$I_{CQ} = 5 \text{ mA}$$

Transistor Parameters

$$\beta = 200$$

$$V_{BE(ON)} = 0.7 \text{ V}$$

$$V_T = 26 \text{ mV}$$

$$V_A = \infty$$


$$a) +V_{BE(ON)} + 2I_{CQ}R_E - V_{CC} = 0 \Rightarrow R_E = \frac{V_{CC} - V_{BE(ON)}}{2I_{CQ}} = \frac{12 - 0.7}{(2)(5\text{mA})} = 1.13 \text{ k}\Omega$$

$$(3) \left. \begin{aligned} V_C &= V_{CC} - R_C I_{CQ} = 12 - (2\text{K})(5\text{mA}) = 2\text{V} \\ V_E &= -V_{BE(ON)} = -0.7\text{V} \end{aligned} \right\} \Rightarrow V_{CE} = 2 - (-0.7) = 2.7\text{V} > V_{CE(SAT)}$$

Forward active ✓

$$b) V_{OQ} = V_{CC} - R_C I_{CQ} = 2\text{V}$$

c) Differential Mode Model:

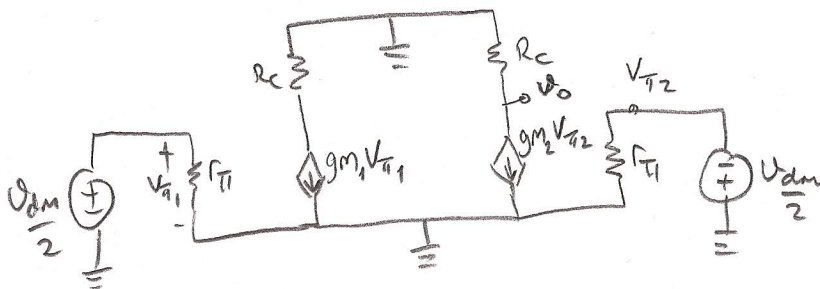

(2)

$$I_{BQ} = \frac{I_{CQ}}{\beta} = \frac{5\text{mA}}{200} = 0.025\text{mA}$$

$$r_{\pi} = \frac{V_T}{I_{BQ}} = \frac{26\text{mV}}{0.025\text{mA}} = 10.4 \text{ k}\Omega$$


$$g_m = \frac{\beta}{r_{\pi}} = \frac{200}{10.4\text{k}} = 19.2 \text{ mA/V}$$

$$v_o = -R_C g_m v_{\pi 2} = -(2\text{K})(19.2\text{mA/V})\left(-\frac{v_{dm}}{2}\right)$$

$$= 19.2 v_{dm} \quad (3)$$

$$\boxed{A_{dm} = 19.2}$$

d) Common-Mode Model:

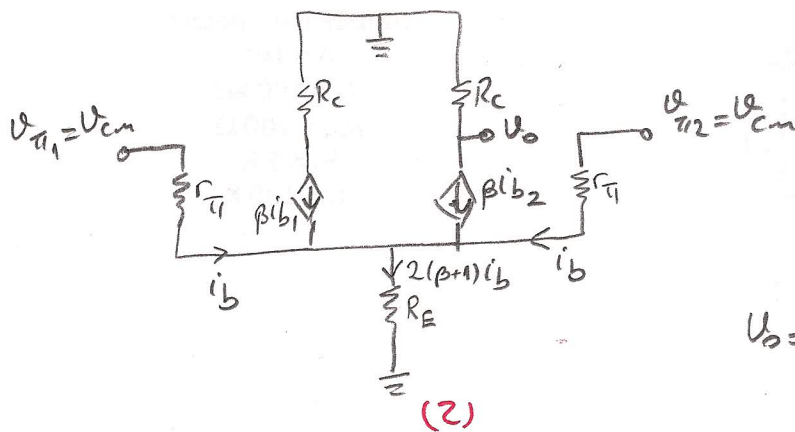

$$i_{b1} = i_{b2} = i_b$$

$$V_{cm} = r_{\pi} i_b + 2(\beta+1) i_b R_E$$

$$= [r_{\pi} + 2(\beta+1) R_E] i_b$$

$$V_o = -\beta R_C i_b = -\frac{\beta R_C}{r_{\pi} + 2(\beta+1) R_E} V_{cm}$$

$$= -\frac{(200)(2k)}{(10.4k) + 2(201)(1.13k)} V_{cm}$$

$$= -\frac{400}{464.66} V_{cm} = -0.86 V_{cm}$$

$$A_{cm} = -0.86$$

e) $CMRR = \left| \frac{A_{dm}}{A_{cm}} \right| = \frac{19.2}{0.86} = 22.3 \Rightarrow CMRR_{dB} = 20 \log(22.3) = 26.97 \text{ dB}$

a) $V_{dm} = V_1 - V_2 = 0.4 \sin(2\pi \times 1000t) \text{ Volts}$


$V_{cm} = \frac{V_1 + V_2}{2} = 2 \sin(2\pi \times 75t) \text{ Volts}$

$$V_o = V_{oQ} + A_{dm} V_{dm} + A_{cm} V_{cm}$$

$$= 2 + (19.2)(0.4 \sin 2\pi \times 1000t) - (0.86)(2 \sin 2\pi \times 75t)$$

$$= 2 + 7.68 \sin 2\pi \times 1000t - 1.72 \sin 2\pi \times 75t \text{ Volts}$$

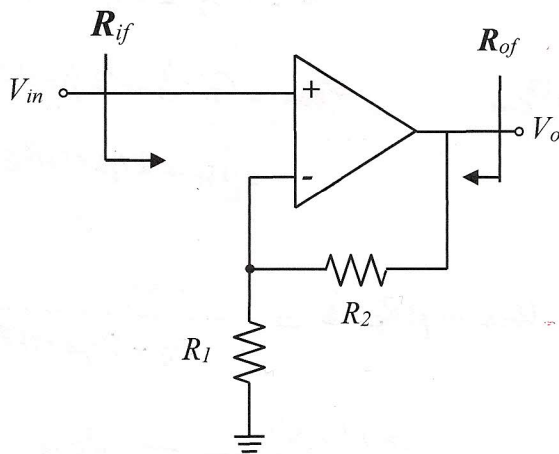Q5. (20 pts) Consider the feedback amplifier given below.



OPAMP Parameters

$$A = 10^3$$

$$R_{in} = 100 \text{ k}\Omega$$

$$R_{out} = 200 \Omega$$




$$R_1 = 1 \text{ K}$$

$$R_2 = 100 \text{ K}$$

- Identify the type of feedback,
- Derive the expressions for the closed loop gain $A_{vf} = v_o/v_{in}$, input resistance R_{if} and output resistance R_{of} .
- Compute the values of the closed loop gain A_{vf} , input resistance R_{if} and output resistance R_{of} .
- Comment on the effect of feedback on the input and output resistances.
- Now, assume OPAMP is ideal ($R_{in} = \infty$ and $R_{out} = 0$) and re-compute the closed loop gain A_{vf} .





a) Series-shunt (3)

b) Feedback circuit model

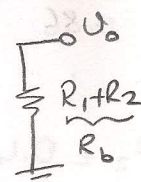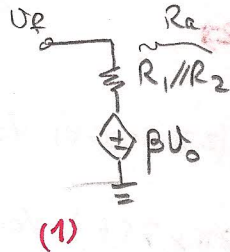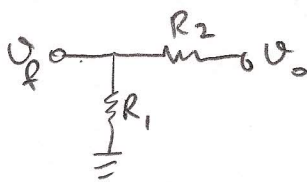

$$\beta = \frac{R_1}{R_1 + R_2} = \frac{1\text{K}}{101\text{K}} \approx 0.01$$

(1)

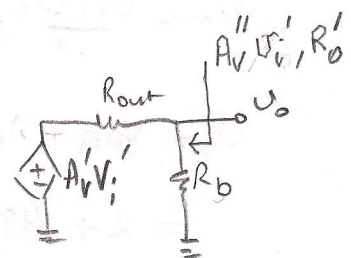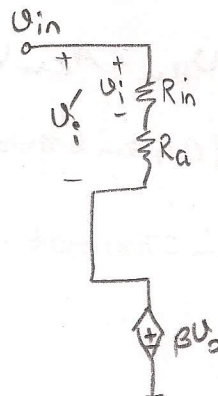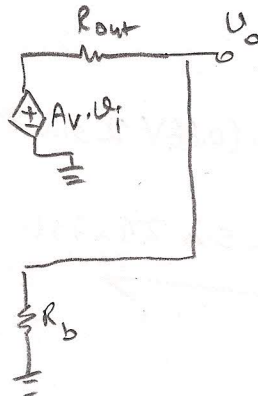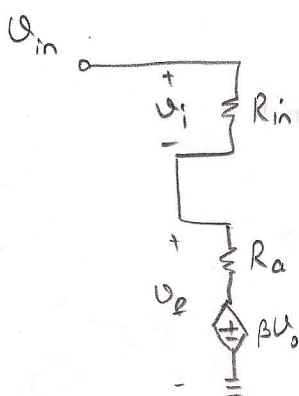


$$R_a = 1\text{K} // 100\text{K} \approx 1\text{K}$$

$$R_b = 1\text{K} + 100\text{K} \approx 101\text{K}\Omega$$

$$V_i = \frac{R_{in}}{R_{in} + R_a} V_i'$$

$$A_v V_i = A_v \frac{R_{in}}{R_{in} + R_a} V_i' = A_v' V_i'$$
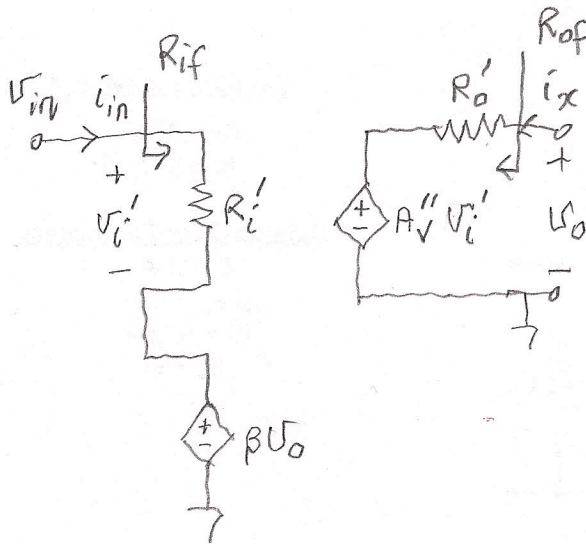
$$A_v' = 10^3 \frac{100}{100+1} = 0.99 \times 10^3$$



$$A''_V U'_i = \frac{R_b}{R_b + R_{out}} \cdot A'_V U'_i$$

$$A''_V = \frac{101K}{101K + 0.2K} \cdot 0.99 \times 10^3 \approx 0.99 \times 10^3$$

$$R'_o = R_b // R_{out} = 101K // 0.2K = 0.2K$$

$$R'_i = R_{in} + R_a = 100K + 1K = 101K$$

$$U_o = A''_V U'_i = A''_V (U_{in} - \beta U_o) = A''_V U_{in} - A''_V \beta U_o$$

$$(1 + A''_V \beta) U_o = A''_V U_{in} \Rightarrow A_{vf} = \frac{U_o}{U_{in}} = \frac{A''_V}{1 + \beta A''_V}$$

$$R_{if} = \frac{U_{in}}{i_{in}} = \frac{U'_i + \beta U_o}{i_{in}} = \frac{U'_i + \beta A''_V U'_i}{i_{in}} = (1 + \beta A''_V) \frac{U'_i}{i_{in}} = (1 + \beta A''_V) R'_i$$

$$R_{of} = \left. \frac{U_o}{i_x} \right|_{U_{in}=0} \quad \left. \begin{aligned} U_o &= R'_o i_x + A''_V U'_i \\ U'_i &= U_{in} - \beta U_o \big|_{U_{in}=0} = -\beta U_o \end{aligned} \right\} \begin{aligned} U_o &= R'_o i_x - A''_V \beta U_o \\ (1 + A''_V \beta) U_o &= R'_o i_x \\ \frac{U_o}{i_x} &= \frac{R'_o}{1 + A''_V \beta} \end{aligned}$$

$$\text{Hence } R_{of} = \frac{R'_o}{1 + A''_V \beta}$$

$$(c) \quad A_{vf} = \frac{A''_V}{1 + \beta A''_V} = \frac{0.99 \times 10^3}{1 + (0.99 \times 10^3)(10^{-2})} = \frac{0.99 \times 10^3}{1 + 9.9} = 90$$

$$R_{if} = (1 + \beta A''_V) R'_i = (1 + 9.9)(101K) = 1.1 M\Omega$$

$$R_{of} = \frac{R'_o}{1 + A''_V \beta} = \frac{0.2K}{1 + 9.9} = 18.3 \Omega$$

(d) Input resistance is increased from 100K to 1.1MΩ, whereas output resistance is decreased from 200Ω to 18.3Ω.

$$(e) \quad R_{in} = \infty, R_{out} = 0$$

$$A''_V = \frac{R_b}{R_b + R_{out}} \quad A'_V = A'_V = \frac{R_{in}}{R_{in} + R_a} \quad A_V = A_V = 10^3$$

$$R_{if} = (1 + \beta A''_V) R'_i = (1 + \beta A_V)(R_{in} + R_a) = \infty$$

$$R_{of} = \frac{R'_o}{1 + \beta A''_V} = \frac{R_b // R_{out}}{1 + \beta A''_V} = 0$$