


LO-4

To Do the Analysis and Design of Power Amplifiers

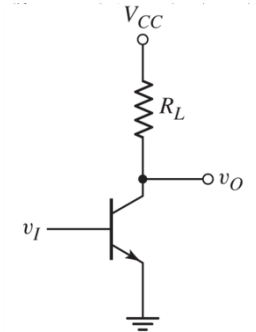1. Consider the common-emitter circuit given in the figure. The circuit parameters are:

$$V_{CC} = 24 \text{ V}, R_L = 8 \Omega.$$

- Determine the maximum current and voltage limits of the BJT transistor.
- For which value of R_L , the power dissipation over transistor is maximum? What is the maximum power dissipation then?




2. Consider the common-source circuit given. The circuit parameters are:

$$V_{DD} = 10 \text{ V}, R_D = 5 \text{ k}\Omega.$$

and the transistor parameters are:

$$V_{TN} = 1 \text{ V}, K_n = 1 \text{ mA/V}^2, \text{ and } \lambda = 0.$$

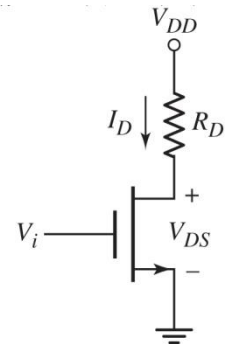
Assume the output voltage is limited to the range between the SAT-LIN transition point and $v_{DS} = 0.9 V_{DD}$ to minimize the nonlinear distortion. Calculate the actual efficiency of this Class A output stage.



3. The maximum current, voltage and power ratings of the power BJT transistor used in the circuit of Q2 are 5 A, 80 V and 25 W respectively. Determine the value of R_D that produces a maximum power in the transistor for (i) $V_{DD} = 80 \text{ V}$ and (ii) $V_{DD} = 50 \text{ V}$.

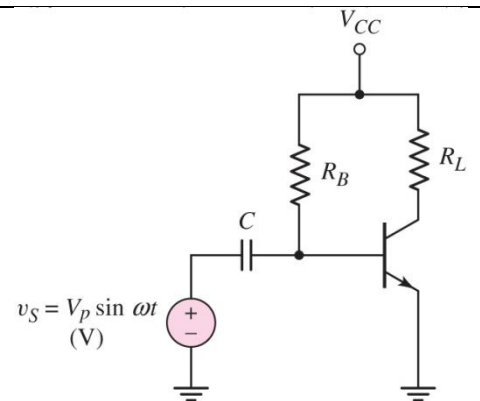4. The common-emitter circuit in the figure is biased at $V_{CC} = 24 \text{ V}$. The maximum transistor power is $P_{D,max} = 20 \text{ W}$ and the current gain $\beta = 80$.

- Determine R_L and R_B such that the maximum power is delivered to the load.
- Find the value of V_p for the input signal that delivers the signal power. State any assumption.




5. Consider the Class-B output stage with complementary MOSFETs shown in the figure. The transistor parameters are:

$$V_{TN} = V_{TP} = 0, K_n = K_p = 0.4 \text{ mA/V}^2.$$


Let $R_L = 5 \text{ k}\Omega$.

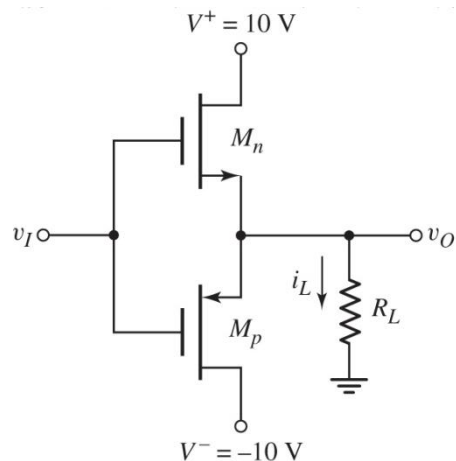- (a) Find the maximum output voltage such that M_n remains biased in the saturation region. What are the corresponding values of i_L and v_I for this condition.
- (b) Determine the conversion efficiency for a symmetrical sine-wave output signal with peak value found in part (a).



6. Consider the class-AB stage in the figure. The diodes and the transistors are matched with parameters $I_S = 6 \times 10^{-12} \text{ A}$, and $\beta = 40$.

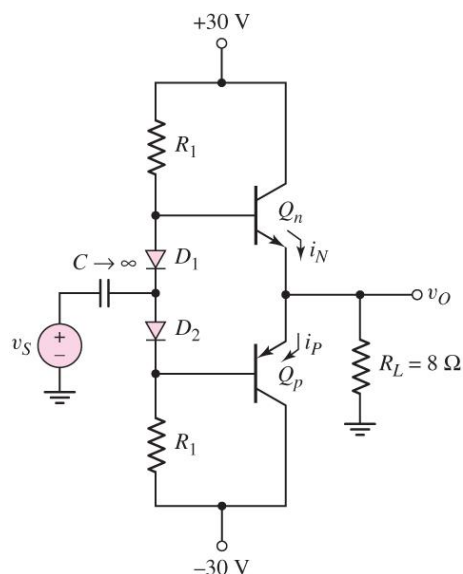- (a) Determine R_1 such that the minimum current in the diodes is 25 mA when $v_O = 24 \text{ V}$. Find i_N and i_P for this condition.
- (b) Using the results of part (a), determine the diode and the transistor currents when $v_O = 0$.




7. Consider the Class B output stage shown in the figure ($V_{CC} = 12 \text{ V}$). Assume the transistors are ideal with


$$V_{BE1} = V_{BE2} = 0 \text{ V}$$

$$V_{CEsat1} = V_{CEsat2} = 0 \text{ V}.$$

The input is a sinusoidal waveform as well as the output as given below.


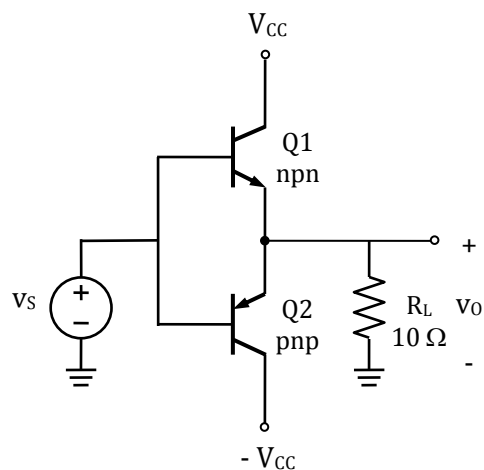
- i) Determine the average power dissipation over the load as a function of V_{CP} .
- ii) Determine the total average power drawn from the sources as a function of V_{CP} .
- iii) The average power dissipation over one transistor as a function of V_{CP} .
- iv) Determine the power conversion efficiency as a function of V_{CP} .



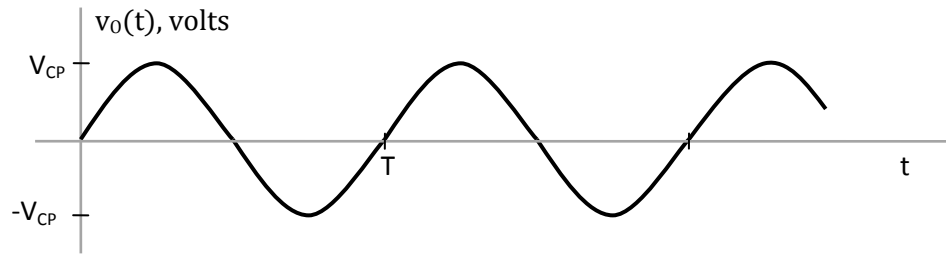


- v) What is the power efficiency when $V_{CP} = 6$ V.
- vi) For which value of V_{CP} , the power efficiency is maximum? What is the maximum power efficiency then?
- vii) For which value of V_{CP} , the power dissipation over any transistor is maximum? What is the maximum power over any transistor then?

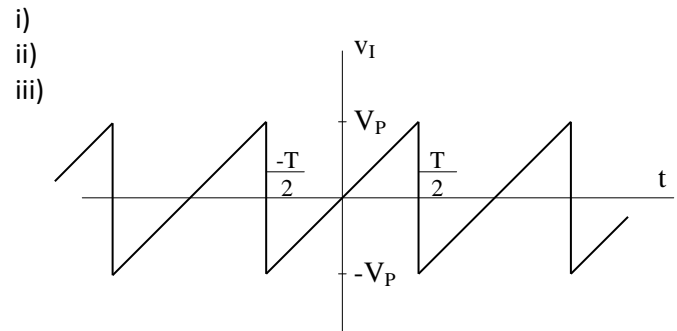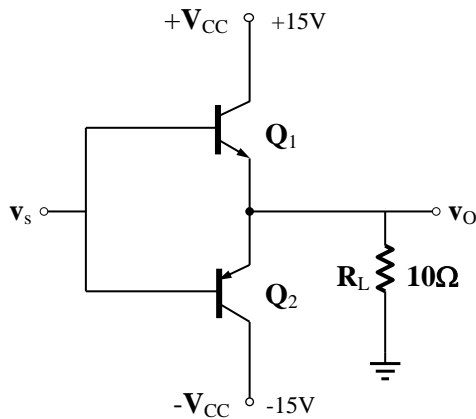8. Consider the power amplifier shown in the figure.



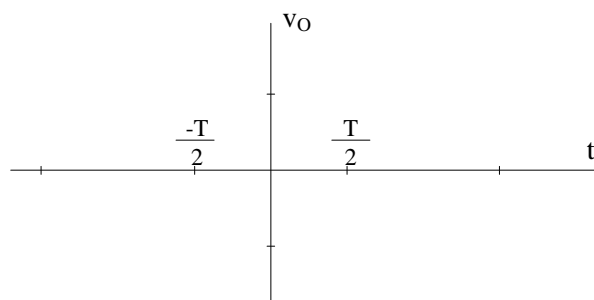- i) Assume the transistors are ideal with $V_{BE1}=V_{BE2}=0$ V and $V_{CEsat1} = V_{CEsat2} = 0$, for the input voltage v_I given above, plot the output waveform. (Assume $V_P < V_{CC}$)



- ii) Determine the average power dissipation over the load as a function of V .
- iii) The total average power drawn from the sources as a function of V .
- iv) The average power dissipation over one transistor as a function of V .
- v) Determine the power conversion efficiency as a function of V .
- vi) For which value of V , the power efficiency is maximum? What is the maximum power efficiency then?
- vii) For which value of V , the power dissipation over each transistor is maximum? What is the maximum power dissipation over any transistor then?