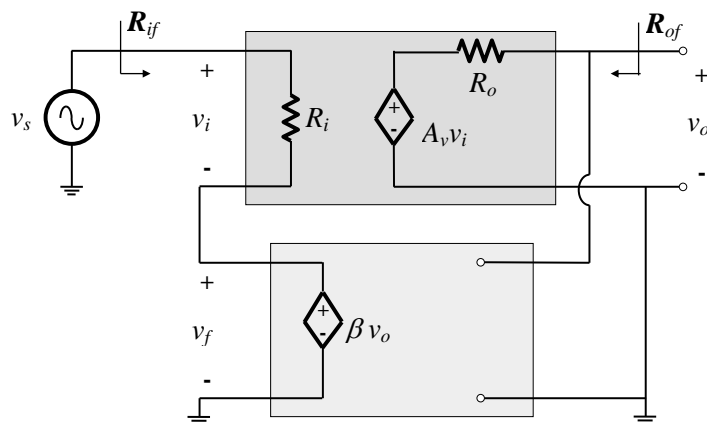


LO-8

To Do the Analysis and Design of Feedback Amplifiers

1. Consider the feedback amplifier given below



$$\begin{aligned} A_{MB} &= 10^4 \\ \omega_H &= 10^4 \text{ rad/sec} \\ R_i &= 100 \text{ k}\Omega \\ R_o &= 100 \Omega \\ \beta &= 0.01 \end{aligned}$$

- Identify the type of feedback,
- Derive the expressions for the closed loop gain $A_{vf} = v_o/v_s$, R_{if} and R_{of} .
- Comment on the effect of feedback on the input and output resistances.
- Derive the closed loop voltage gain $G_v(j\omega)$ and determine the bandwidth, assuming $\beta=0.01$, independent of frequency, and

$$A_v(j\omega) = \frac{A_{MB}}{1 + \frac{j\omega}{\omega_H}}$$

- Find and compare the gain-bandwidth products of the basic amplifier and the feedback amplifier.

2. Consider the feedback amplifier given in Q1. The negative-feedback amplifier has a closed-loop gain of $A_{vf} = 100$ and an open-loop gain $A_v = 10^5$. If a manufacturing error results in a reduction of A_v to 10^3 , what closed-loop gain results? What is the percentage change in A_{vf} corresponding to this factor of 100 reduction in A_v ?


3. Consider the voltage amplifier given in the figure. The op-amp parameters are:

$$A_v = 5 \times 10^3, R_i = 10 \text{ k}\Omega, \text{ and } R_o = 1 \text{ k}\Omega.$$

and the transistor parameters are

$$\beta = 100 \text{ and } V_A = 80 \text{ V.}$$

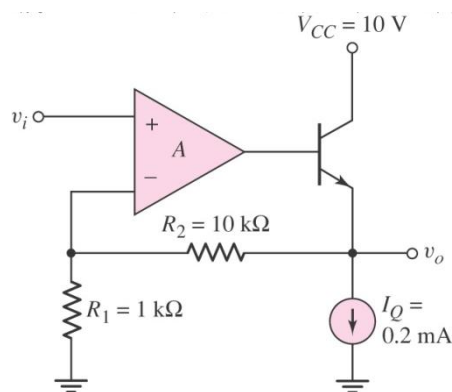Determine $A_{vf} = v_o/v_s$, R_{if} and R_{of} .



4. The circuit shown on the right is an ac equivalent of circuit of a feedback amplifier.

The transistor parameters are:

$$\beta = 100 \text{ and } V_A = \infty.$$


The quiescent collector currents are:

$$I_{C1} = 14.3 \text{ mA}, I_{C2} = 4.62 \text{ mA}, \text{ and } I_{C3} = 4.47 \text{ mA}.$$

- (a) Determine the closed loop voltage gain

$$A_{vf} = v_o/v_s$$

- (b) Determine R_{if} and R_{of} .

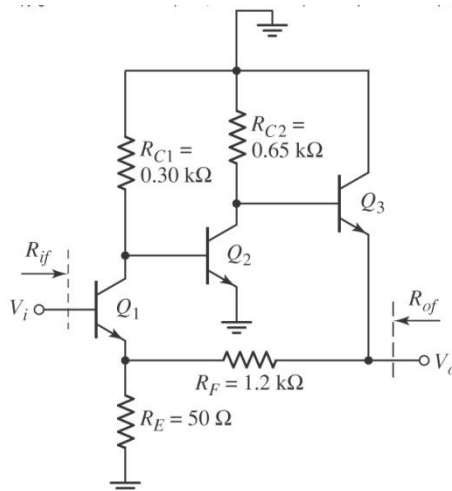

5. A basic source follower is given in the figure. Assume the transistor is biased such that $I_{DQ} = 0.5 \text{ mA}$ and let $R_S = 2 \text{ k}\Omega$.


Assume the transistor parameters are:

$$V_{TN} = 1 \text{ V}, \lambda = 0.$$

- (a) If the conduction parameter is $K_n = 0.5 \text{ mA/V}^2$, determine


$$A_{vf} = v_o/v_s, \text{ and } R_{of}.$$

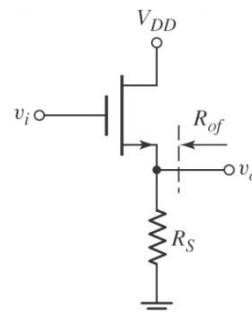- (b) Determine the percentage change in A_{vf} and R_{of} if the conduction parameter increases to $K_n = 0.8 \text{ mA/V}^2$.




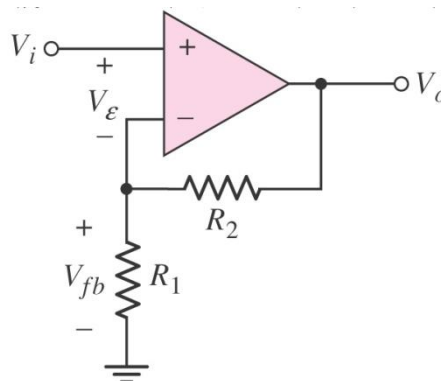6. Consider the noninverting op-amp in the given figure with $R_i = 50 \text{ k}\Omega$, $R_1 = 10 \text{ k}\Omega$, $R_2 = 90 \text{ k}\Omega$ and $A_v = 10^4$.


Determine $A_{vf} = v_o/v_i$, R_{if} and R_{of} .



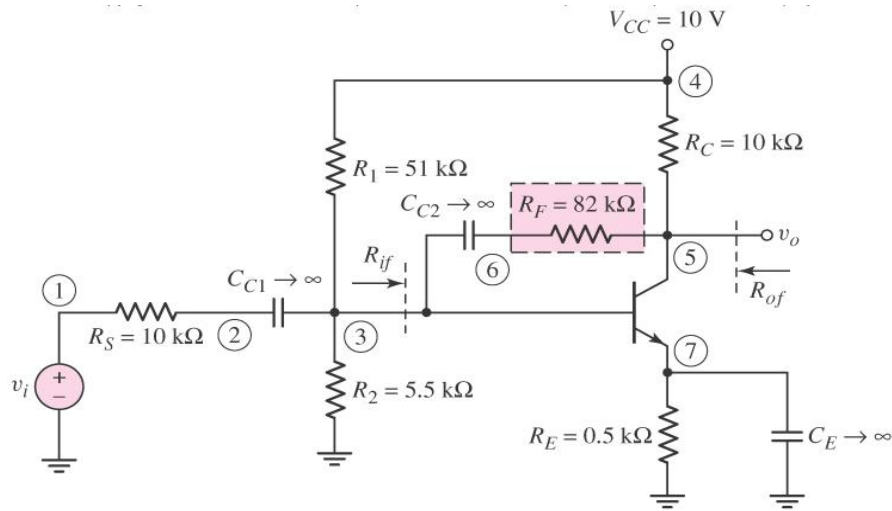7. Consider the amplifier given below. The transistor parameters are $\beta = 100$, $V_{BE(on)} = 0.7$ V, and $V_A = \infty$. Determine the transresistance and voltage gain.




(a)

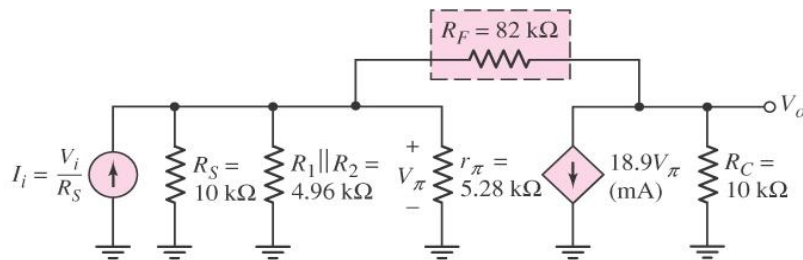

(b)

8. Determine the voltage gain of the feedback amplifier given in Q7 using Miller's Theorem.

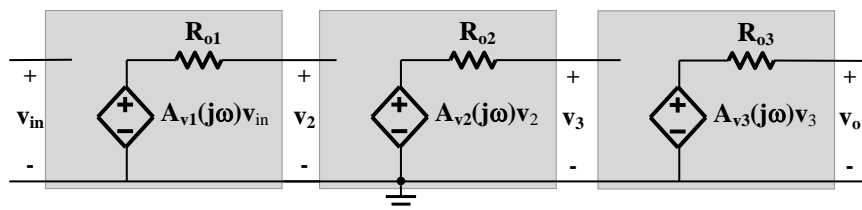9. Consider the following voltage amplifier having 3 stages.



The voltage gain of the stages are given as follows:

$$A_{v1}(j\omega) = \frac{10}{1 + j(\omega/\omega_1)}; \quad A_{v2}(j\omega) = \frac{100}{1 + j(\omega/\omega_2)}; \quad A_{v3}(j\omega) = \frac{100}{1 + j(\omega/\omega_3)};$$

where $\omega_1 = 10^6$ rad/sec, $\omega_2 = 10^7$ rad/sec, $\omega_3 = 10^9$ rad/sec,


- a) Plot the Bode plot of the overall voltage gain

$$A_v(j\omega) = \frac{V_o(j\omega)}{V_{in}(j\omega)}$$

- b) Plot the phase of the overall gain as a function of the frequency.

[Hint: For $\omega = 10^8$ rad/sec, $\tan^{-1}(\omega/10^7) + \tan^{-1}(\omega/10^9) \cong 90^\circ$]

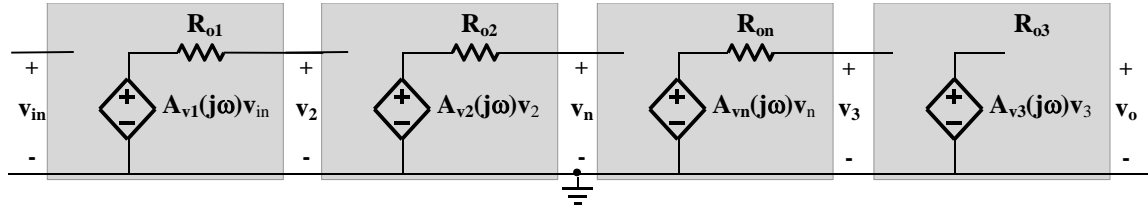- c) If the above amplifier is to be used in a feedback circuit having a constant $\beta=0.1$, is the overall amplifier stable? Determine the critical frequency ω_c where the amplifier is unstable.
- d) The amplifier is modified by adding a new stage as shown below.



The voltage gain of the new stage is

$$A_n(j\omega) = \frac{1 + j(\omega/\omega_1)}{1 + j(\omega/\omega'_1)}$$

For $\omega'_1=10^4$ rad/sec, is the overall feedback amplifier stable?

- a) Determine the phase and gain margins of the feedback amplifier ($\beta=0.1$) with this new modified amplifier, graphically. [Hint: $\log(3.16) = 0.5$, $\tan^{-1}(3.16) = 72^\circ$]

