



EEE 331

Analog Electronics

Prof. Dr. Murat Aşkar

A-420


E-mail: askar@ieu.edu.tr

Web: <http://homes.ieu.edu.tr/maskar/>




Analog and Digital Signals

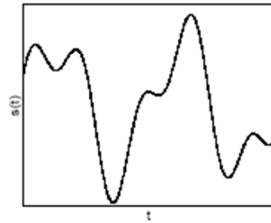
Continuous-time, continuous-valued
(analog) signal




Discrete-time, continuous-valued signal

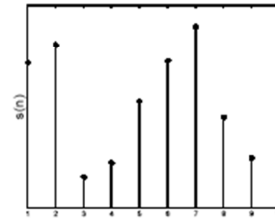

Continuous-time, discrete-valued signal

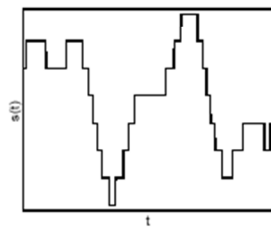


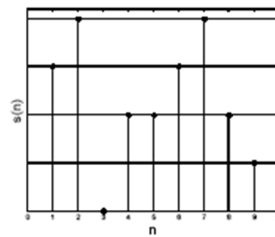Discrete-time, discrete-valued
(digital) signal






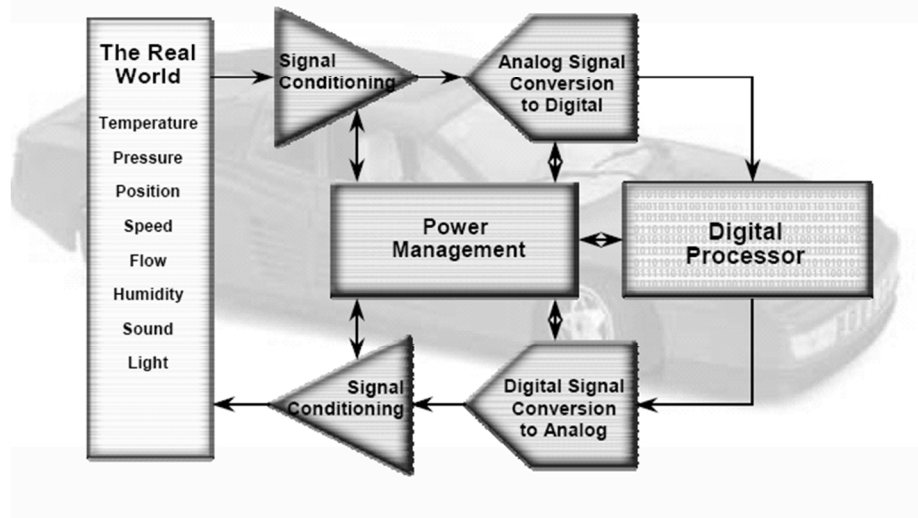
Analog Signals are links to the real world



Transceiver

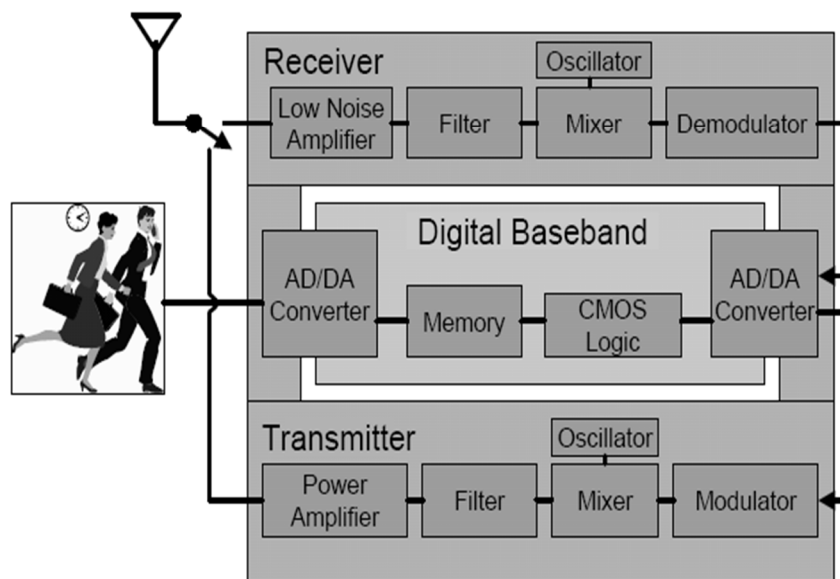

Bio-eng: Neuronal implants

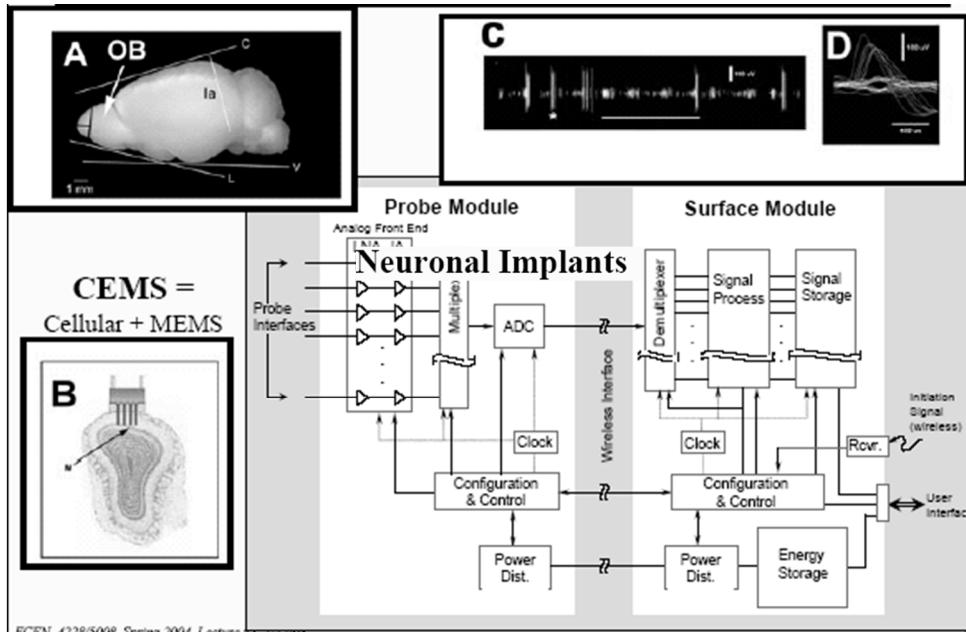




Linear Amplifiers (1)

Multiply amplitude of a signal by a constant scalar quantity



$$x_o(t) = A x_i(t)$$

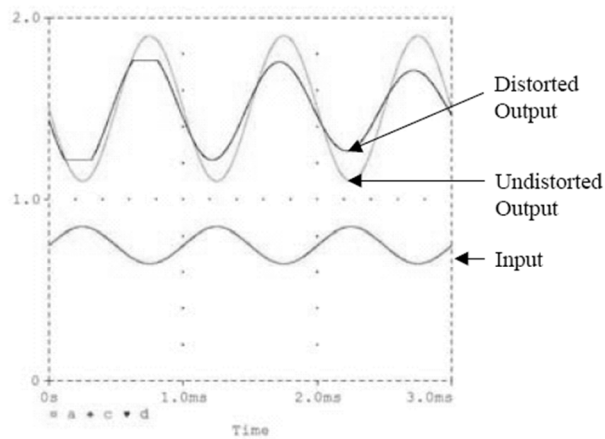

Non-scalar or
non-uniform
amplification
is called
distortion

Linear Amplifiers (2)

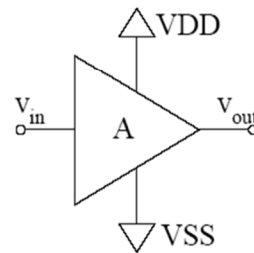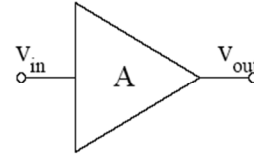
- Symbol for a single-ended input linear voltage amplifier.
- Ideally provides linear voltage gain regardless of the amplitude of the input signal
- Real amplifiers have power supplies that limit the amplitude of the output
- If input is too large, output clamps






Transfer Characteristics (1)

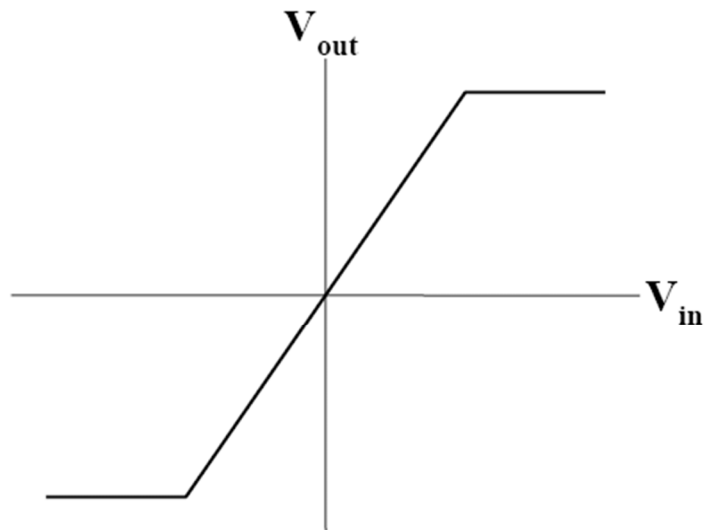Plot of amplifier output versus amplifier input




Transfer Characteristics (2)

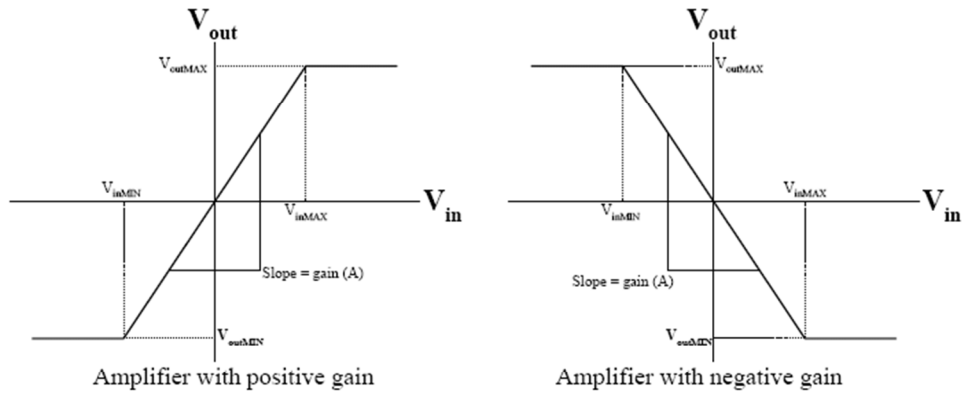

- Gain = Slope
- To operate amplifier in its linear region, the input must be kept small enough


Real Transfer Characteristics

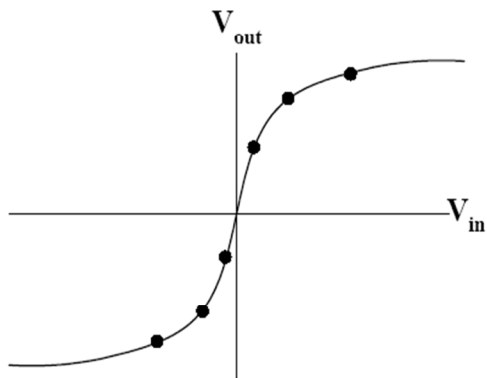

- Each circle represents a different DC component for the input and output signals – called an **operating point**
- Location of **operating point** has an effect on
 - input signal range
 - amplifier gain magnitude
 - amount of distortion


Operating Point (1)

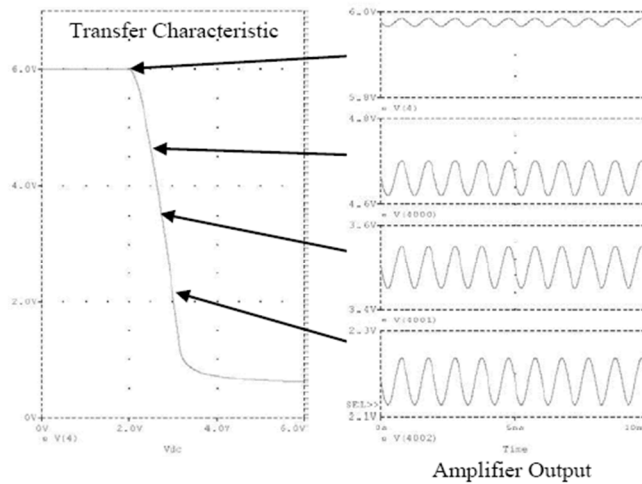Voltage gain, output DC voltage, allowable input magnitude range are affected



Operating Point (2)

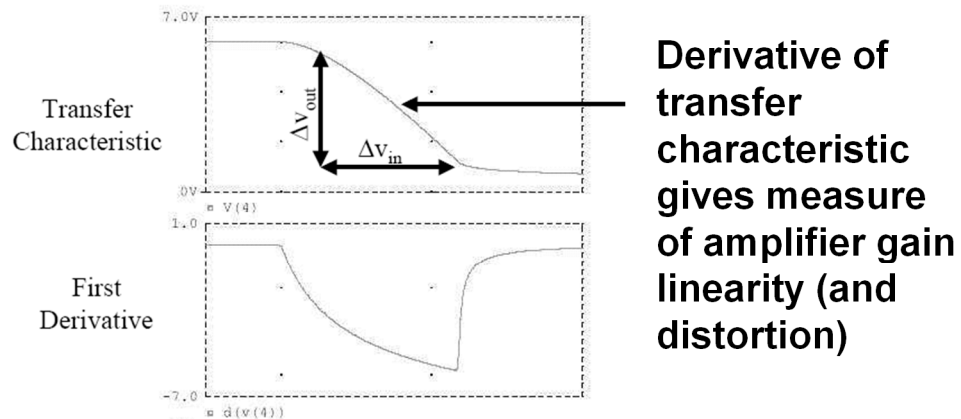Input and output signal amplitude ranges are maximized when operating point is near middle of linear region





Signal Convention (1)


- **DC** magnitudes in uppercase symbol and subscript
 - Example: I_D , V_D
- **Ac signal** quantities in lowercase symbol & subscript
 - Example: $i_d(t)$, $v_d(t)$
- Total **DC + ac signal** quantities in lowercase symbol, uppercase subscript
 - Example: $i_D(t)$, $v_D(t)$

Signal Convention (2)

In general

$$v_D(t) = V_D + v_d(t)$$

$$i_C(t) = I_C + i_c(t)$$

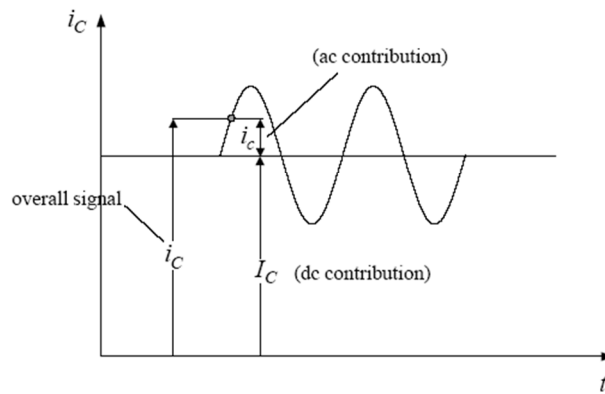



Superposition


- If the amplifier is linear, **superposition** can be applied. Each component can be determined separately.
- Determine the **DC magnitude** of the output using DC model (i.e capacitors are open circuited, inductors are short circuited)
 - Example: I_O , V_O
- Determine the **ac signal component** of the output using the ac model (i.e., DC sources are killed and capacitors are short circuited, inductors are open circuited) as
 - Example: $v_o(t) = A_v v_i(t)$




Amplifier Classification

Input	Output	Type
Voltage	Voltage	Voltage
Voltage	Current	Transconductance
Current	Voltage	Transresistance
Current	Current	Current


Ideal Voltage Amplifier

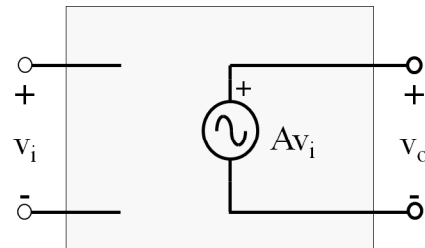

Real Voltage Amplifier

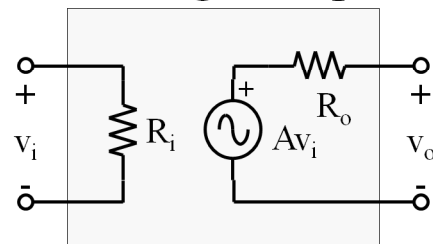


Loaded Ideal Voltage Amplifier

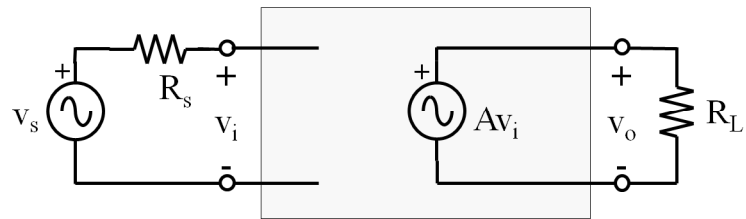


$$\frac{V_o}{V_s} = A$$

Loaded Voltage Amplifier

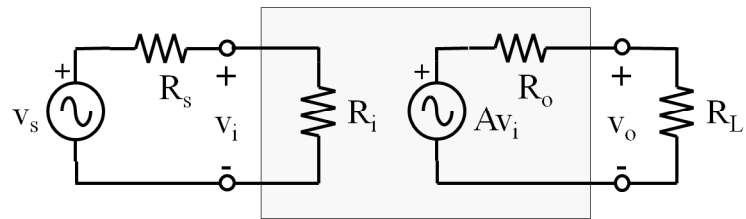


$$\frac{v_o}{v_s} = A \frac{R_i}{R_s + R_i} \frac{R_L}{R_o + R_L}$$


Ideal Current Amplifier

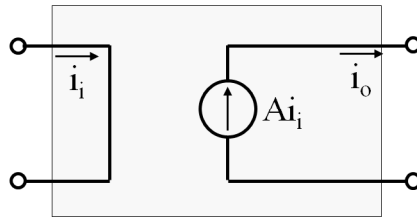

Real Current Amplifier

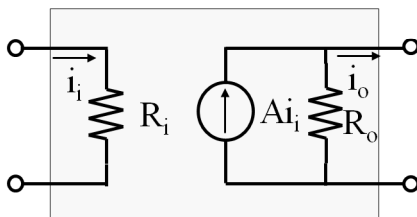


Loaded Ideal Current Amplifier

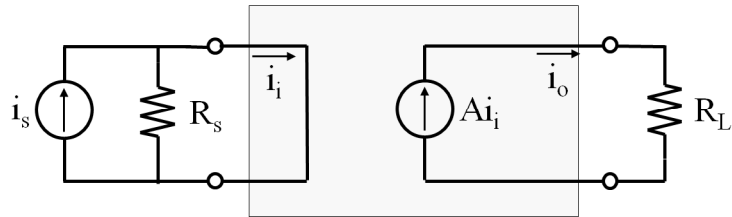


$$\frac{i_o}{i_s} = A$$

Loaded Current Amplifier

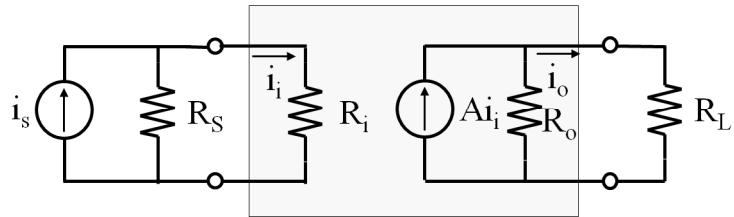


$$\frac{i_o}{i_s} = A \frac{R_s}{R_s + R_i} \frac{R_o}{R_o + R_L}$$

To determine Input Resistance R_i

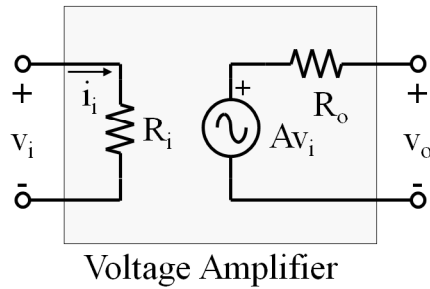

Voltage Amplifier

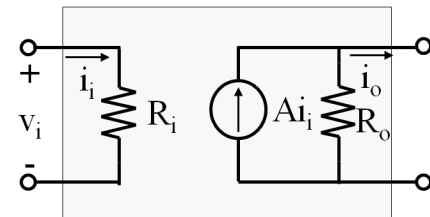- Apply input voltage v_i (or input current i_i)
- Determine the input current i_i (or input voltage v_i)




Current Amplifier

Then

$$R_i = v_i / i_i$$

To determine Output Resistance R_o

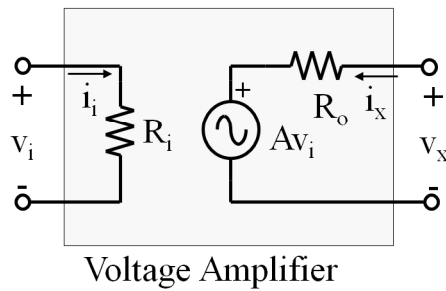

- Kill the input signal (set v_i or i_i to zero)
- Apply a test voltage v_x to the output node
- Determine the current i_x that the source delivers to the circuit

Then

$$R_o = v_x / i_x$$

