

EXPERIMENT 8

NMOS Differential Amplifier

A. Background

A differential amplifier designed using NMOS transistors is shown below in Fig. 8.1. The biasing is provided through the resistor R_0 .

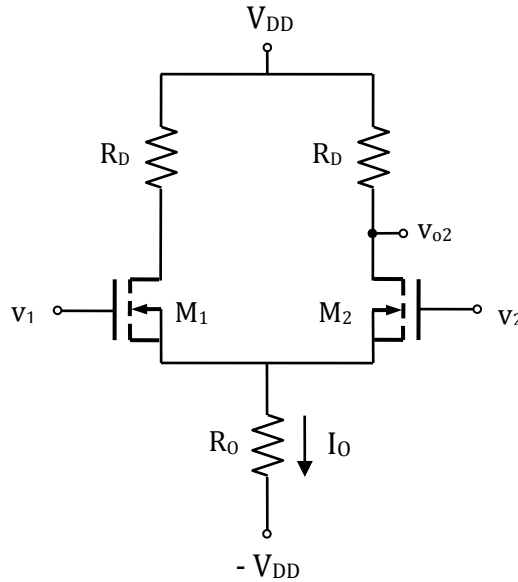


Fig. 8. 1. NMOS DC Circuit

The transistors M_1 and M_2 are assumed matched with identical parameters. The currents I_{D1} and I_{D2} are equal and

$$I_{D1} = I_{D2} = I_0/2$$

Defining two new signals v_{cm} and v_{dm} as:

$$v_{cm} = \frac{v_1 + v_2}{2}$$

and

$$v_{dm} = v_1 - v_2$$

The inputs v_1 and v_2 may be expressed as:

$$v_1 = v_{cm} + \frac{v_{dm}}{2}$$

and

$$v_2 = v_{cm} - \frac{v_{dm}}{2}$$

Using superposition the output is expressed as:

$$v_{o2} = A_{cm2} v_{cm} - A_{dm2} v_{dm}$$

where

$$A_{cm2} = \frac{-g_m R_D}{1+2g_m R_o} \text{ and } A_{dm2} = \frac{g_m R_D}{2}$$

The common mode ratio is defined as:

$$CMRR = \frac{A_{dm2}}{A_{cm2}}$$

Or in dB

$$CMRR_{dB} = 20 \log \left(\frac{A_{dm2}}{A_{cm2}} \right)$$

B. Preliminary Work

- a) Consider the NMOS differential amplifier given in Fig. 8.2. Assume $V_{DD} = 12$ V. Determine the value of R_o to set the current $I_o = 1$ mA, using the transistor parameters obtained in Experiment 2.

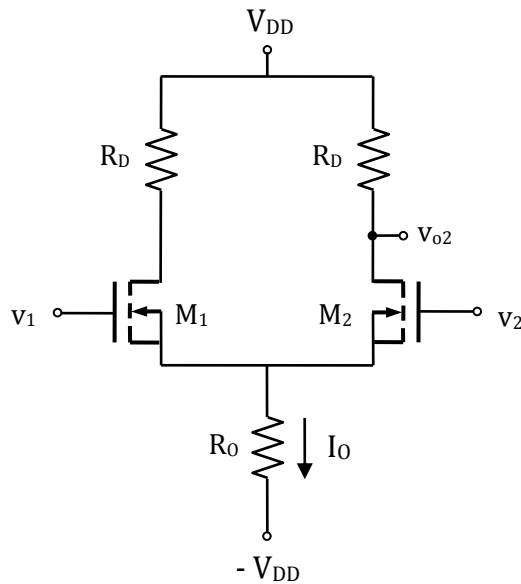


Fig. 8. 2. NMOS Differential Amplifier

- b) Determine the value of R_D to set $V_{DSQ} = 8$ V.

C. Experimental Work

1. Set up the circuit given in Fig. 8.3. with $V_{DD} = 12\text{ V}$, $R_o = 10\text{ k}\Omega$, $R_D = 3.9\text{ k}\Omega$.

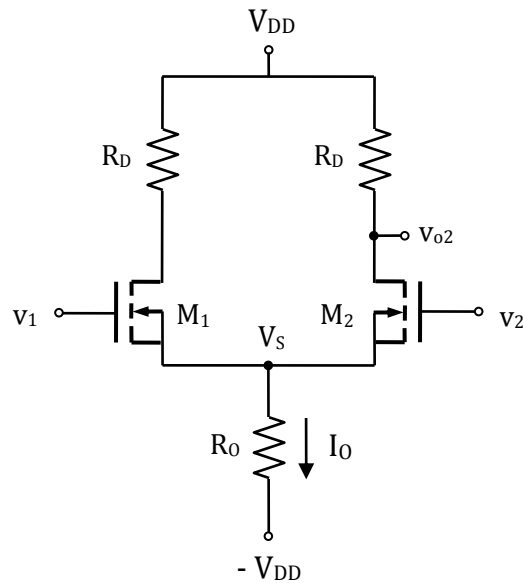


Fig. 8. 3. NMOS Differential Amplifier

2. Set $v_1 = v_2 = 0$. Measure the voltage V_S and the current I_O . Also measure V_{DSQ} .
3. Make necessary modifications to set the current $I_O \cong 1\text{ mA}$ and $V_{DSQ} \cong 8\text{ V}$.
4. Now apply a sinusoidal input $v_1 = v_2 = V_P \sin \omega_0 t$ at $f_0 = 1\text{ kHz}$. Determine A_{cm2} .
5. Apply $v_1 = V_P \sin \omega_0 t$ at $f_0 = 1\text{ kHz}$ and $v_2 = 0$. Determine A_{dm2} .
6. Calculate CMRR.